

AERO | ASTRO



# 16.682 - Prototyping Avionics Spring 2006

LECTURE 3

February 15, 2006

DEPARTMENT OF AERONAUTICS AND ASTRONAUTICS

**Alvar Saenz-Otero**

# Outline

- **More on Components**
  - **Resistors, Capacitors, Inductors: ideal vs. real**
  - **First and second order systems**
  - **Diodes**
- **Amplifiers**

# Last time...

- **Four component laws**

- $v = iR$

- $i = C \frac{dv}{dt}$

- $v = L \frac{di}{dt}$


- $P = iv = i^2 R = \frac{v^2}{R}$

- **Two network laws**

- **KCL - Kirchoff's Current Law**

$$\sum i_n = 0$$

In/out of node

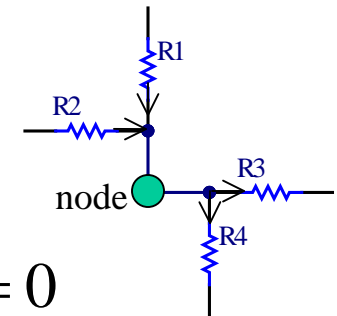


$$i_1 + i_2 + i_3 + i_4 = 0$$

- **KVL - Kirchoff's Voltage Law**

$$\sum v_n = 0$$

Around a loop

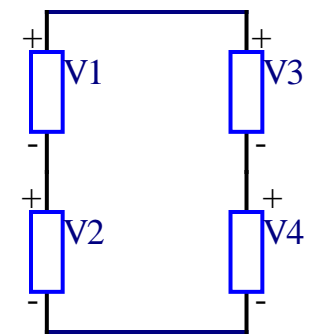

$$V_1 + V_2 = V_3 + V_4$$

# Ideal vs. Real

- **Ideal**

- **Wire**

- $R=0, C=0, L=0$




- **Resistor**

- $C=0, L=0$



- **Capacitor**

- $R=0, L=0$

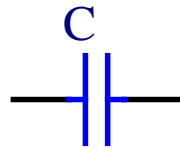


- **Inductor**

- $R=0, C=0$



- **Real**


- $R \neq 0, C \neq 0, L \sim 0$

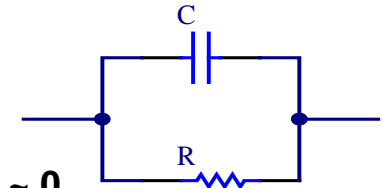


- $C \sim 0, L \sim 0$



- $R \neq 0, L \sim 0$

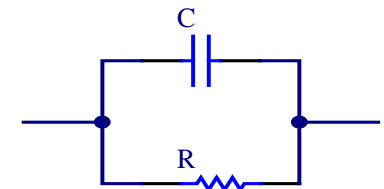


- $R \neq 0, C \sim 0$

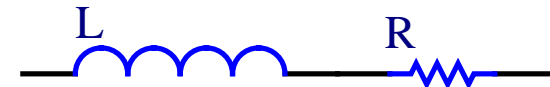


# Review of Resistors

- Serial

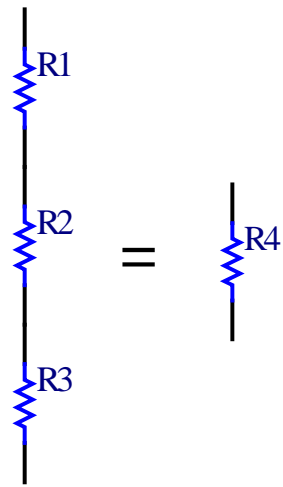

$$R_1 + R_2 + R_3 = R_4$$

- Parallel

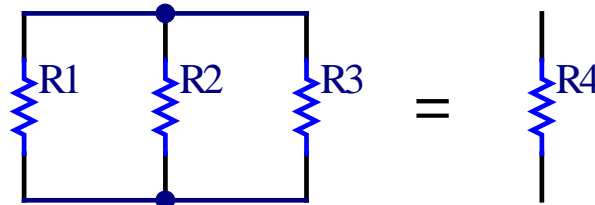


$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{R_4}$$

- For two resistors

$$R_4 = \frac{R_1 R_2}{R_1 + R_2}$$


- Voltage divider

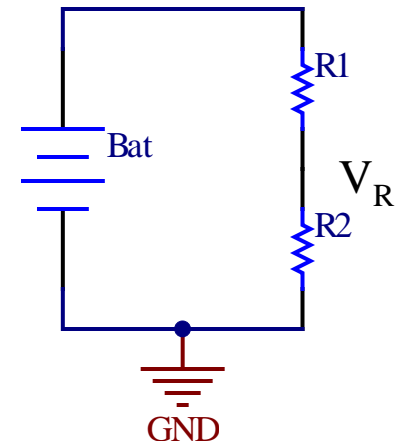

$$V_R = V_{Bat} \frac{R_2}{R_1 + R_2}$$


# First Order Systems

- Relation of different inputs



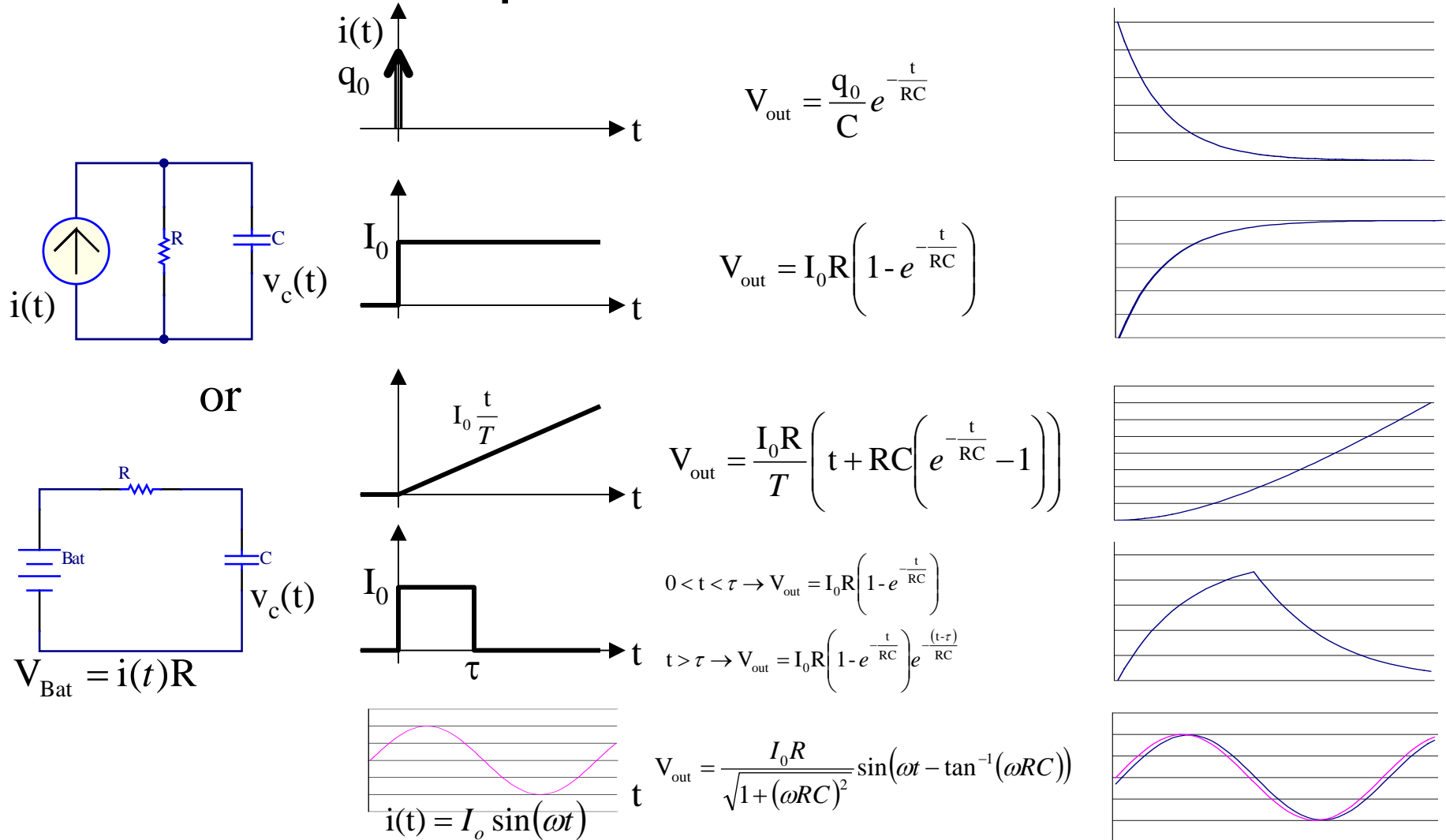

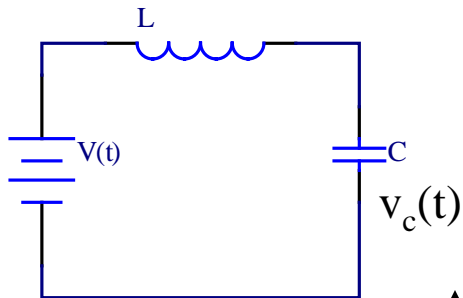
# Second Order Systems


- Circuits that combine capacitors and inductors are higher order


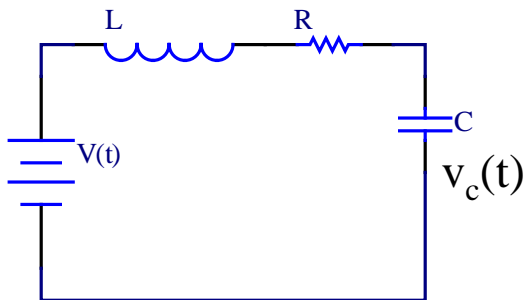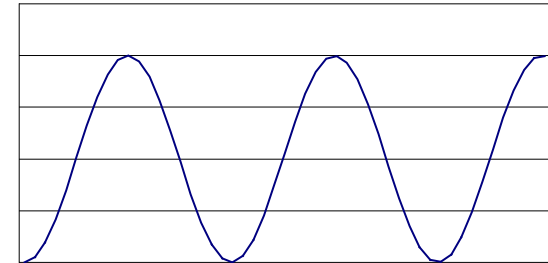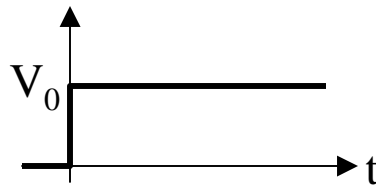
$$V_{\text{out}} = V_0(1 - \cos(\omega_0 t))$$
$$\omega_0 = \frac{1}{\sqrt{LC}}$$



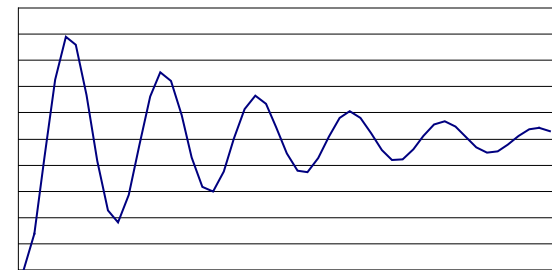
$$V_{\text{out}} \approx V_0(1 - \cos(\omega_0 t)) \cdot e^{-\xi t}$$
$$\omega_0 = \frac{1}{\sqrt{LC}}, \xi = \frac{R}{2L}$$



**Resistor adds dampening**



# Diodes

- **Ideal**

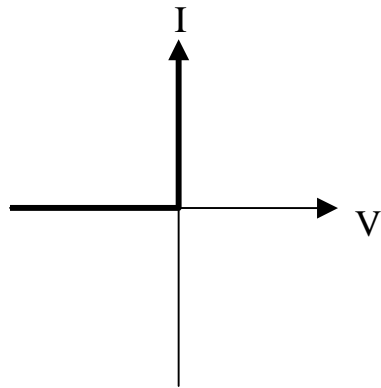

- Does not allow current flow when voltage is reversed
  - Stops all current
- Allows infinite current flow when positive voltage is applied

- **Real**

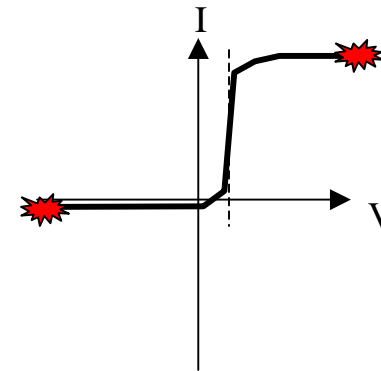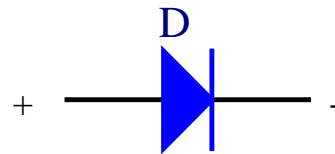


- Voltage drop: minimum voltage before current can go through
- Current leak: small amount of current goes through in reverse
- Maximum/Minimum voltage in both forward and reverse
- Maximum current in forward


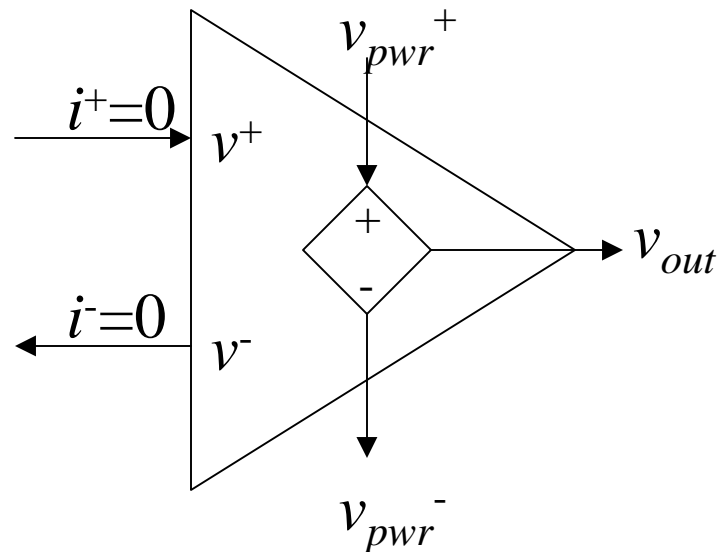
# Introduction to Operational Amplifiers

- Utilize an “external” power source to amplify/modify an input signal
  - Allow the use of feedback to closely track the signal



- Adjusts the output voltage  $V_{out}$  to try make  $v^+$  and  $v^-$  be the same
  - The user adds elements (wires, resistors, capacitors, etc) which create current loops between the output and inputs to create feedback loops