


6.002 Demo# 17A (Load Set up demo#17A)
Integrator and Differentiator RC Network
Lecture 20

Agarwal Fall 2000

Purpose: This demo shows how an RC circuit can approximate either an integrator (capacitor voltage at high frequencies) or a differentiator (resistor voltage at low frequencies).

Steps:

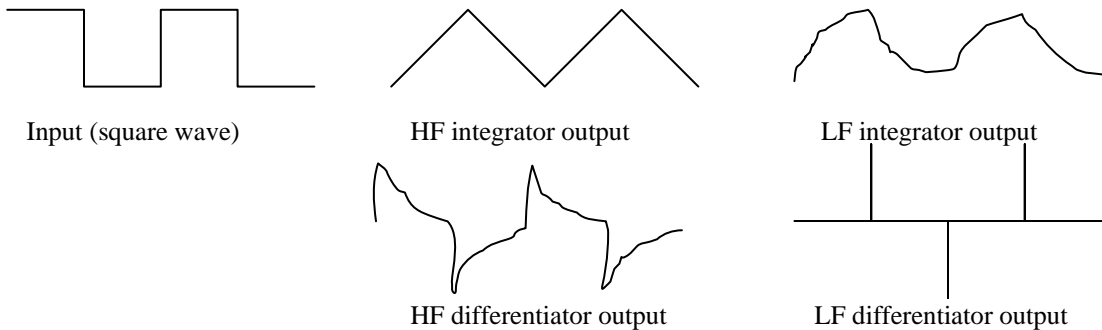1. Show the differentiator input (square wave) and output (resistor voltage) at a low frequency (100 Hz). Note the output looks like the derivative of the input.
2. Increase the frequency (1 kHz, then 10 kHz), adjusting the scope accordingly. Note that the output begins to look less like a derivative and more like the decaying exponential response.
3. Show the integrator input (square wave) and output (capacitor voltage) at a high frequency (10 kHz). Note the output looks like the integral of the input.
4. Decrease the frequency (1 kHz, then 100 Hz), adjusting the scope accordingly. Note that the output begins to look less like an integral and more like the decaying exponential step response.



Description: To show Integrator and Differentiator, using RC Network.

For Differentiator set the switch on the card to Differentiator.

For Integrator set the switch on the card to Integrator.

For Differentiator use the following frequencies:

100 HZ, 1000 HZ and 10,000 HZ

For Intregator use the following frequencies:

10,000 HZ, 1000 HZ and 100 HZ

Make sure you monitor the input (square wave)

See schematic diagram next page for more detail

Oscilloscope Setup

CH	V/DIV	OFFSET	MODE	FUNC	MATH	VERTICAL	HORIZONTAL
1 on	2	-3.5	DC	off			
2 on	2	2.8	DC	off			
3 on	2	1.3	DC	off			
4 off			DC	off			

Horizontal: 5 ms

Acquisition: AUTO AUTO 4

Trigger: CH1

Waveform Generator Setup

Power Supply Setup

UNIT	WAVE	AMP	OFFSET	FREQ	+6	+25	-25	OUTPUT
					off	off	off	
<hr/>								
FG1 Square		1*	0	100 & 1000 & 10,000 HZ !				Trigger: INT

- Amplitude depends on the Prof.!
- ! See above for integrator frequencies set up

6.002 Demo #17A
Integrator and Differentiator RC Network. Prof. Lang Spring 99

