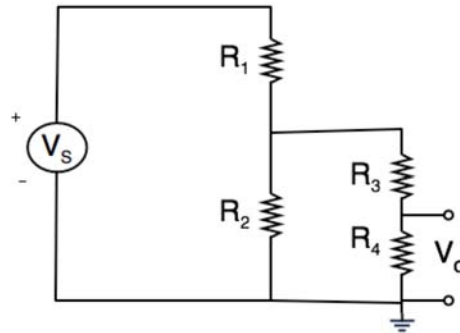


## Problem Wk.9.3.4: Thevenin divider


This problem considers how to use Thevenin equivalents to analyze the combination of two resistor divider circuits.

1. Consider the following circuit:



Assume that  $R_1 = R_2 = R_3 = R_4$ , what is the ratio  $V_o/V_S$ ?

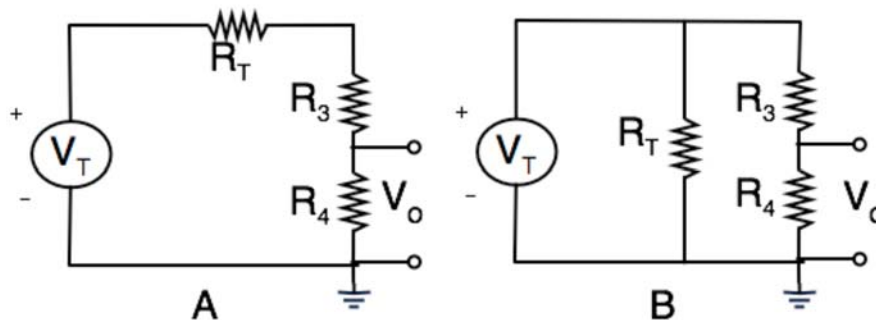2. Let's replace the part of the circuit including the voltage source and  $R_1$  and  $R_2$  with its Thevenin equivalent (whose output terminals connect to  $R_3$  and ground). The resulting circuit is one of these two circuits:



All four answers below must be entered before checking. All four answers will be marked incorrect when checked until all four answers are entered correctly.

Assume that  $V_S = 10$  and all the resistors are 1000 Ohm.

Which circuit is the correct one? (Enter A or B):

What is the Thevenin voltage source  $V_T$ ? (Enter float)  Volt.

What is the value of the Thevenin resistance  $R_T$ ? (Enter float)  Ohm.

What is the value of  $V_o$ ? (Enter float)  Volt.

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.01SC Introduction to Electrical Engineering and Computer Science  
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.