


### 6.01: Introduction to EECS I

#### Circuits

March 15, 2011
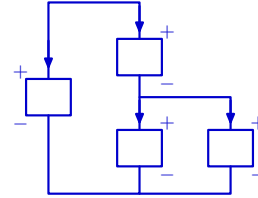
#### The Circuit Abstraction

- Circuits represent systems as connections of elements
- through which currents (through variables) flow and
  - across which voltages (across variables) develop.



#### The Circuit Abstraction


We can represent the flashlight as a voltage source (battery) connected to a resistor (light bulb).



The voltage source generates a voltage  $v$  across the resistor and a current  $i$  through the resistor.
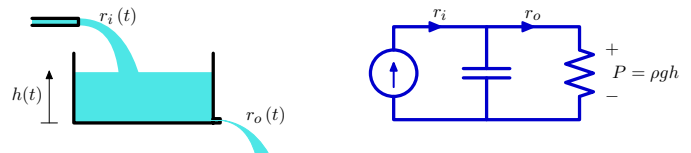
#### The Circuit Abstraction

We can represent the flow of water by a circuit.



Flow of water into and out of tank are represented as “through” variables  $r_i$  and  $r_o$ , respectively. Hydraulic pressure at bottom of tank is represented by the “across” variable  $P = \rho gh$ .


#### The Circuit Abstraction

Circuits are important for two very different reasons:

- as **physical systems**
  - power (from generators and transformers to power lines)
  - electronics (from cell phones to computers)
- as **models** of complex systems
  - neurons
  - brain
  - cardiovascular system
  - hearing
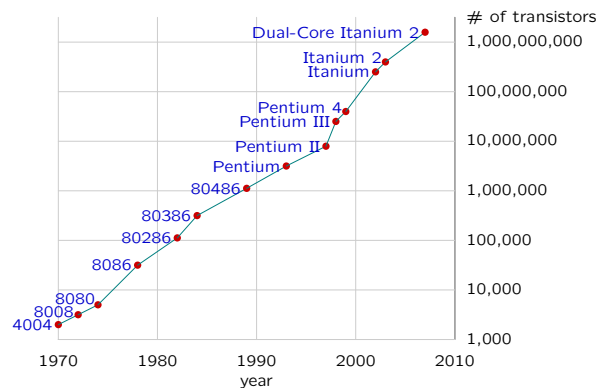
#### The Circuit Abstraction



Circuits are basis of enormously successful semiconductor industry.



What design principles enable development of such complex systems?

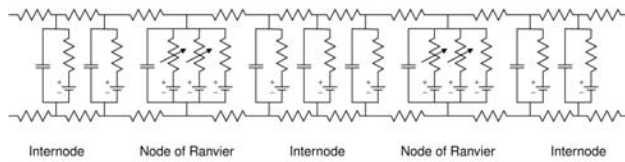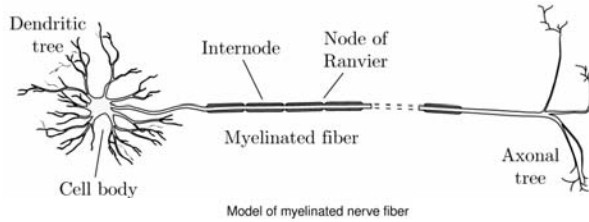**The Circuit Abstraction**

Circuits as models of complex systems: myelinated neuron.




Model of myelinated nerve fiber

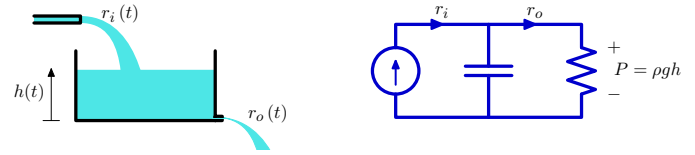**The Circuit Abstraction**

**Circuits** represent systems as connections of elements

- through which currents (through variables) flow and
- across which voltages (across variables) develop.



The **primitives** are the elements:


- sources,
- capacitors, and
- resistors.

The **rules of combination** are the rules that govern

- flow of current (through variable) and
- development of voltage (across variable).

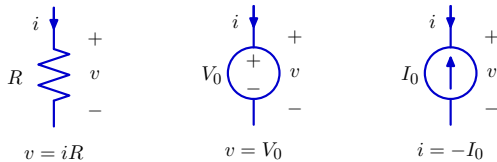**Analyzing Circuits: Elements**


We will start with the simplest elements: resistors and sources



**Analyzing Simple Circuits**


Analyzing simple circuits is straightforward.

Example 1:

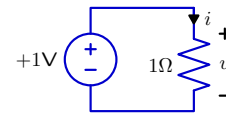

The voltage source determines the voltage across the resistor,  $v = 1V$ , so the current through the resistor is  $i = v/R = 1/1 = 1A$ .


Example 2:

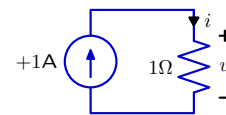

The current source determines the current through the resistor,  $i = 1A$ , so the voltage across the resistor is  $v = iR = 1 \times 1 = 1V$ .

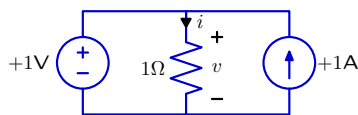**Check Yourself**

What is the current through the resistor below?




1. 1A
2. 2A
3. 0A
4. cannot determine
5. none of the above

**Analyzing More Complex Circuits**

More complex circuits can be analyzed by systematically applying Kirchhoff's voltage law (KVL) and Kirchhoff's current law (KCL).

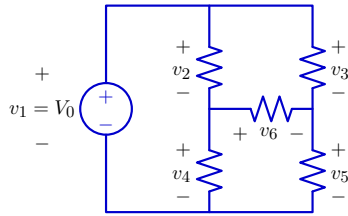
**Analyzing Circuits: KVL**

KVL: The sum of the voltages around any closed path is zero.



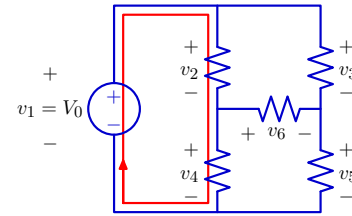**Analyzing Circuits: KVL**

KVL: The sum of the voltages around any closed path is zero.




Example:  $-v_1 + v_2 + v_4 = 0$  or equivalently  $v_1 = v_2 + v_4$ .

How many other KVL relations are there?

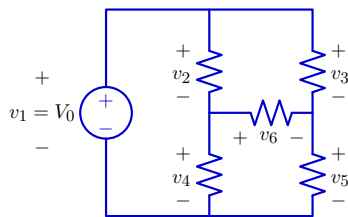**Check Yourself**


How many KVL equations can be written for this circuit?



- 1. 3
- 2. 4
- 3. 5
- 4. 6
- 5. 7

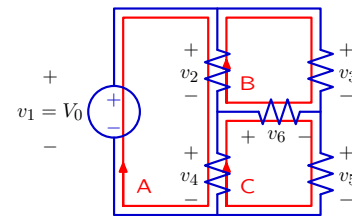**Analyzing Circuits: KVL**


Planar circuits can be characterized by their "inner" loops. KVL equations for the inner loops are independent.



- A :  $-v_1 + v_2 + v_4 = 0$
- B :  $-v_2 + v_3 - v_6 = 0$
- C :  $-v_4 + v_6 + v_5 = 0$

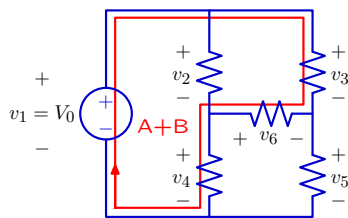**Analyzing Circuits: KVL**

All possible KVL equations for planar circuits can be generated by combinations of the "inner" loops.



- A :  $-v_1 + v_2 + v_4 = 0$
- B :  $-v_2 + v_3 - v_6 = 0$
- A+B :  $-v_1 + v_2 + v_4 - v_2 + v_3 - v_6 = -v_1 + v_3 - v_6 + v_4 = 0$

**KVL: Summary**

The sum of the voltages around any closed path is zero.


One KVL equation can be written for every closed path in a circuit.

Sets of KVL equations are not necessarily linearly independent.

KVL equations for the "inner" loops of planar circuits are linearly independent.

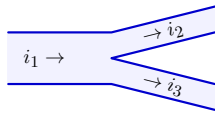**Kirchhoff's Current Law**

The flow of electrical current is analogous to the flow of incompressible fluid (e.g., water).




Current  $i_1$  flows into a **node** and two currents  $i_2$  and  $i_3$  flow out:

$$i_1 = i_2 + i_3$$

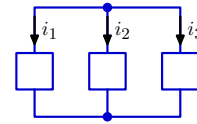**Kirchhoff's Current Law**

The net flow of electrical current into (or out of) a **node** is zero.




Here, there are two nodes, each indicated by a dot.

The net current out of the top node must be zero:

$$i_1 + i_2 + i_3 = 0.$$

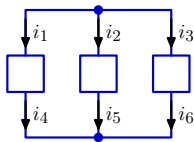**Kirchhoff's Current Law**

Electrical currents cannot accumulate in elements, so current that flows into a circuit element must also flow out.



$$i_1 = i_4$$

$$i_2 = i_5$$


$$i_3 = i_6$$

Since  $i_1 + i_2 + i_3 = 0$  it follows that

$$i_4 + i_5 + i_6 = 0.$$

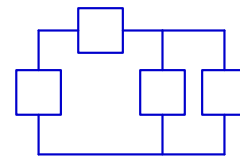**Check Yourself**


How many linearly independent KCL equations can be written for the following circuit?



- 1. 1
- 2. 2
- 3. 3
- 4. 4
- 5. 5

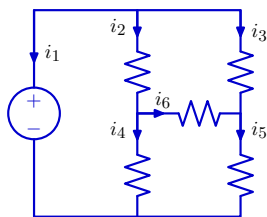**Check Yourself**


How many distinct KCL relations can be written for this circuit?



- 1. 3
- 2. 4
- 3. 5
- 4. 6
- 5. 7

**Analyzing Circuits: KCL**

The net current out of any closed surface (which can contain multiple nodes) is zero.

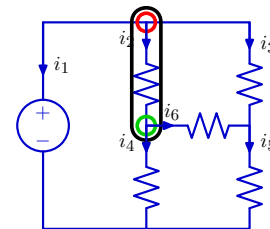


node 1:  $i_1 + i_2 + i_3 = 0$

node 2:  $-i_2 + i_4 + i_6 = 0$

nodes 1+2:  $i_1 + i_2 + i_3 - i_2 + i_4 + i_6 = i_1 + i_3 + i_4 + i_6 = 0$

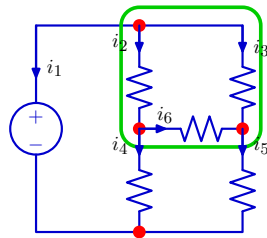**Analyzing Circuits: KCL**

The net current out of any closed surface (which can contain multiple nodes) is zero.



nodes 1+2:  $i_1 + i_3 + i_4 + i_6 = 0$   
 node 3:  $-i_3 - i_6 + i_5 = 0$   
 nodes 1+2+3:  $i_1 + i_3 + i_4 + i_6 - i_3 - i_6 + i_5 = i_1 + i_4 + i_5 = 0$   
 Net current out of nodes 1+2+3 = net current into bottom node!


**KCL: Summary**

The sum of the currents out of any node is zero.  
 One KCL equation can be written for every closed surface (which contain one or more nodes) in a circuit.  
 Sets of KCL equations are not necessarily linearly independent.  
 KCL equations for every primitive node except one (ground) are linearly independent.

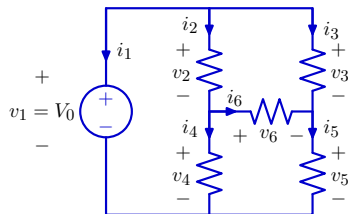**KVL, KCL, and Constitutive Equations**


Circuits can be analyzed by combining

- all linearly independent KVL equations,
- all linearly independent KCL equations, and
- one constitutive equation for each element.



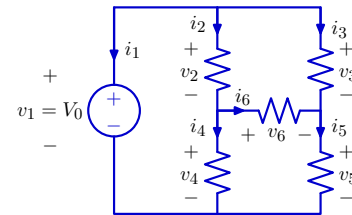**KVL, KCL, and Constitutive Equations**

Unfortunately, there are a lot of equations and unknowns.




12 unknowns:  $v_1, v_2, v_3, v_4, v_5, v_6, i_1, i_2, i_3, i_4, i_5$  and  $i_6$ .  
 12 equations: 3 KVL + 3 KCL + 5 for resistors + 1 for V source  
 This circuit is characterized by 12 equations in 12 unknowns!

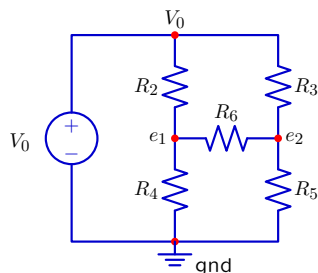**Node Voltages**

The "node" method is one (of many) ways to systematically reduce the number of circuit equations and unknowns.

- label all nodes except one: ground (gnd)  $\equiv$  0 volts
- write KCL for each node whose voltage is not known




KCL at  $e_1$ :  
 $\frac{e_1 - V_0}{R_2} + \frac{e_1 - e_2}{R_6} + \frac{e_1}{R_4} = 0$   
 KCL at  $e_2$ :  
 $\frac{e_2 - V_0}{R_3} + \frac{e_2 - e_1}{R_6} + \frac{e_2}{R_5} = 0$

- solve (here just 2 equations and 2 unknowns)

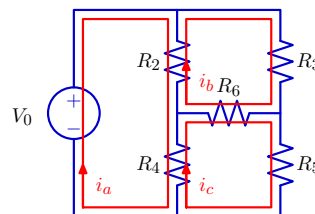**Loop Currents**

The "loop current" method is another way to systematically reduce the number of circuit equations and unknowns.

- label all the loop currents
- write KVL for each loop



loop a:  
 $-V_0 + R_2(i_a - i_b) + R_4(i_a - i_c) = 0$   
 loop b:  
 $R_2(i_b - i_a) + R_3(i_b) + R_6(i_b - i_c) = 0$   
 loop c:  
 $R_4(i_c - i_a) + R_6(i_c - i_b) + R_5(i_c) = 0$

- solve (here just 3 equations and 3 unknowns)

**Analyzing Circuits: Summary**

We have seen three (of many) methods for **analyzing** circuits. Each one is based on a different set of variables:


- currents and voltages for each element
- node voltages
- loop currents

Each requires the use of all constitutive equations.

Each provides a systematic way of identifying the required set of KVL and/or KCL equations.

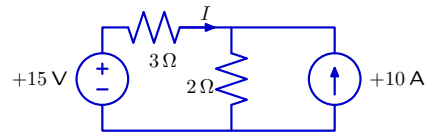**Check Yourself**

Determine the current  $I$  in the circuit below.




1. 1 A
2.  $\frac{5}{3}$  A
3. -1 A
4. -5 A
5. none of the above

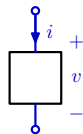**Common Patterns**

Circuits can be simplified when two or more elements behave as a single element.


A "one-port" is a circuit that can be represented as a single element.



A one-port has two terminals. Current enters one terminal (+) and exits the other (-), producing a voltage ( $v$ ) across the terminals.

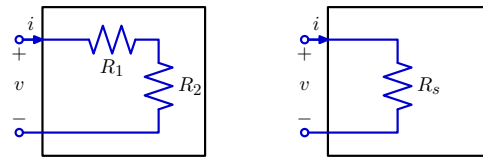**Series Combinations**

The series combination of two resistors is equivalent to a single resistor whose resistance is the sum of the two original resistances.



$$v = R_1 i + R_2 i$$


$$v = R_s i$$

$$R_s = R_1 + R_2$$

The resistance of a series combination is always **larger** than either of the original resistances.

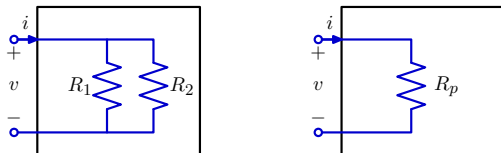**Parallel Combinations**

The parallel combination of two resistors is equivalent to a single resistor whose conductance ( $1/\text{resistance}$ ) is the sum of the two original conductances.



$$i = \frac{v}{R_1} + \frac{v}{R_2}$$


$$i = \frac{v}{R_p}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2} \rightarrow R_p = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} \equiv R_1 || R_2$$

The resistance of a parallel combination is always **smaller** than either of the original resistances.

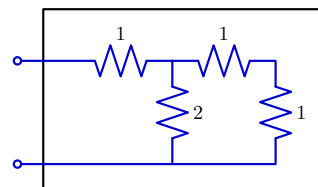**Check Yourself**


What is the equivalent resistance of the following one-port.



1. 0.5
2. 1
3. 2
4. 3
5. 5

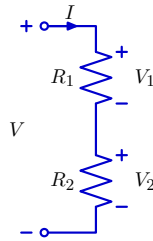**Voltage Divider**

Resistors in series act as voltage dividers.




$$I = \frac{V}{R_1 + R_2}$$

$$V_1 = R_1 I = \frac{R_1}{R_1 + R_2} V$$

$$V_2 = R_2 I = \frac{R_2}{R_1 + R_2} V$$

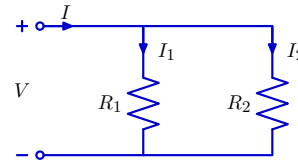**Current Divider**


Resistors in parallel act as current dividers.



$$V = (R_1 || R_2) I$$

$$I_1 = \frac{V}{R_1} = \frac{R_1 || R_2}{R_1} I = \frac{1}{R_1} \frac{R_1 R_2}{R_1 + R_2} I = \frac{R_2}{R_1 + R_2} I$$

$$I_2 = \frac{V}{R_2} = \frac{R_1 || R_2}{R_2} I = \frac{1}{R_2} \frac{R_1 R_2}{R_1 + R_2} I = \frac{R_1}{R_1 + R_2} I$$

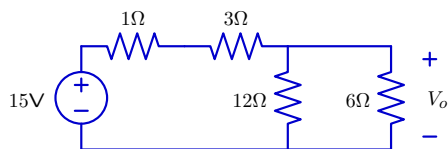**Check Yourself**

Which of the following is true?

1.  $V_o \leq 3\text{V}$
2.  $3\text{V} < V_o \leq 6\text{V}$
3.  $6\text{V} < V_o \leq 9\text{V}$
4.  $9\text{V} < V_o \leq 12\text{V}$
5.  $V_o > 12\text{V}$

**Summary****Circuits** represent systems as connections of elements

- through which currents (through variables) flow and
- across which voltages (across variables) develop.

We have seen three (of many) methods for **analyzing** circuits. Each one is based on a different set of variables:

- currents and voltages for each element
- node voltages
- loop currents

We can simplify analysis by recognizing common **patterns**:

- series and parallel combinations
- voltage and current dividers

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.01SC Introduction to Electrical Engineering and Computer Science  
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.