

DEPARTMENT OF ELECTRICAL ENGINEERING AND COMPUTER SCIENCE
MASSACHUSETTS INSTITUTE OF TECHNOLOGY
 CAMBRIDGE, MASSACHUSETTS 02139

FEEDBACK

THE GOLDEN RULES OF OP-AMPS

(From Horowitz & Hill, page 177)

1. Assuming the op-amp open loop voltage gain $[A_{VOL}]$ is so high that a fraction of a millivolt between the input terminals will swing the output over its full range; we can ignore that small voltage and state golden rule one:

The output attempts to do whatever is necessary to make the voltage difference between the inputs zero.

Note: This does not mean that the op-amp actually changes the voltage at its input. What it does is “look” at its input terminals and swing its output terminal around so that the external feedback network brings the input differential to zero whenever possible.

2. Assuming that op-amps draw very little AC input current (nanoamps to picoamps), we round this down and state:

The inputs draw no current.

Note: They must have some DC current or the op-amp won't work, so a corollary to this rule is that you must ALWAYS provide a DC current path to both inputs.

BENEFITS OF FEEDBACK

STABILIZE GAIN AGAINST DEVICE VARIATIONS, TEMPERATURE, AGING	REDUCE DISTORTION BY THE FEEDBACK FACTOR $[1+\beta A_{ol}]$
MANIPULATE INPUT AND OUTPUT IMPEDANCES BY FEEDBACK FACTOR $[1+\beta A_{ol}]$	INCREASE BANDWIDTH BY THE FEEDBACK FACTOR $[1+\beta A_{ol}]$ [βA_{ol} is often called the LOOP GAIN]

TYPICAL FEEDBACK FACTOR FOR 741 $[A_{ol} = 100,000]$

A=60 dB =1000; $\beta=0.001$; $[1+\beta A_{ol}] = 101$	A=40 dB =100; $\beta=0.01$; $[1+\beta A_{ol}] = 1001$
A=20 dB = 10; $\beta=0.1$; $[1+\beta A_{ol}] = 10,001$	A=10 dB = 3.16; $\beta=0.32$; $[1+\beta A_{ol}] = 31,622$
A=0 dB = 1; $\beta=1$; $[1+\beta A_{ol}] = 100,001$	

DISADVANTAGES OF FEEDBACK

LOSS OF GAIN; NEED MORE STAGES	GREATER TENDENCY TO OSCILLATE
--------------------------------	-------------------------------