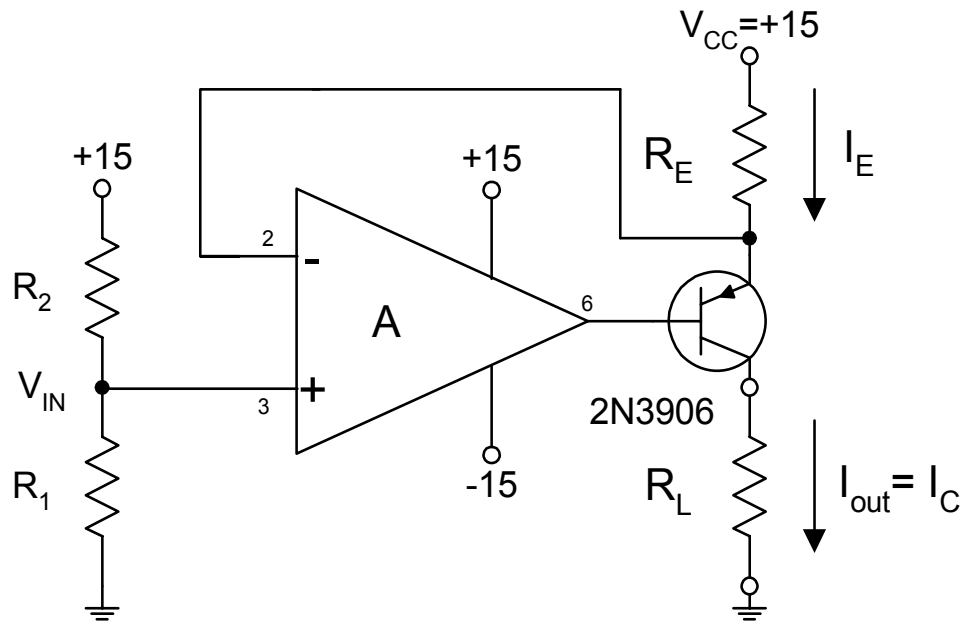


## VOLTAGE-CONTROLLED CURRENT SOURCE [VCCS]



1. Feedback forces  $[+15\text{V} - V_{IN}]$  across  $R_E$ , because  $V_+$  must equal  $V_-$ .
2. If we ignore any offset voltage at the output of the op-amp, the only error comes from the emitter current not quite being equal to the collector current [due to  $I_B$ ]. One can use a Darlington transistor or a JFET to reduce or remove this error.
3. This version of the VCCS does not work if  $V_{IN}$  is an external voltage not referenced to  $V_{CC}$ .
4. Example:  $R_E = 100\Omega$ ,  $\beta_F = 100$ ,  $V_{IN} = 5\text{ V}$ ,  $10\text{ V}$ , and  $14\text{ V}$ :  
 $[15\text{V}-5\text{V}] / 100\Omega = 100\text{ mA}$  for  $I_E$ ;  $I_C = 99\text{ mA}$ .  
 $[15\text{V}-10\text{V}] / 100\Omega = 50\text{ mA}$  for  $I_E$ ;  $I_C = 49.5\text{ mA}$ .  
 $[15\text{V}-14\text{V}] / 100\Omega = 10\text{ mA}$  for  $I_E$ ;  $I_C = 9.9\text{ mA}$ .
5.  $R_1 - R_2$  can of course be a potentiometer for ease of adjustment!