


Consider an inductor connected to a battery with emf \mathcal{E} and a resistor R . At $t = 0$, the switch is closed. Immediately after the switch is closed the current in the circuit is equal to

1. \mathcal{E}/R

2. $2\mathcal{E}/R$


3. Zero

4. Don't have a clue

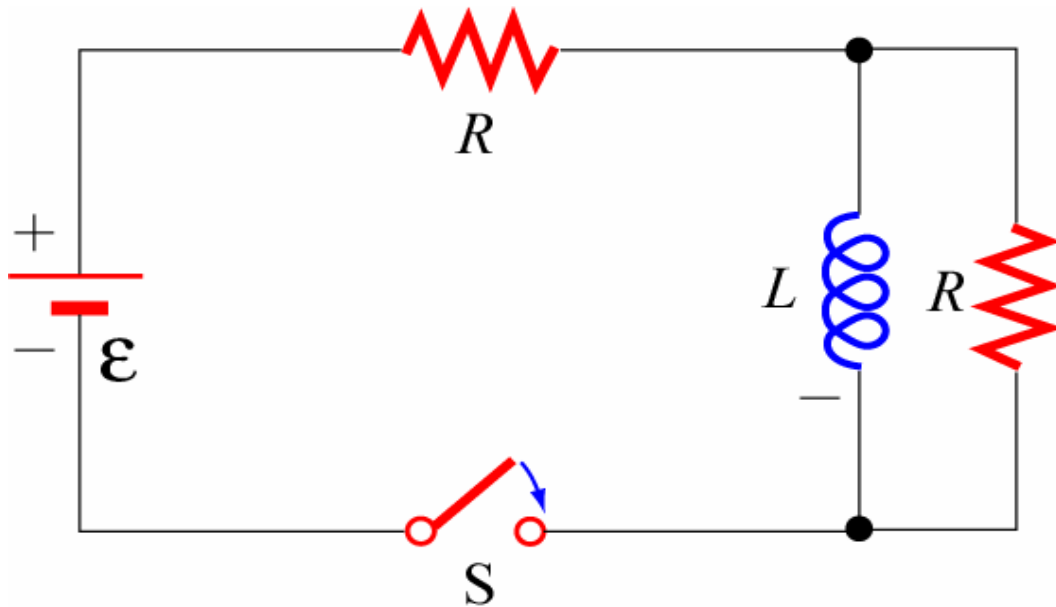


Consider the above circuit, in which the switch S has been closed a very long time. At $t = 0$, the switch is opened. Immediately after the switch is opened the current in the inductor is equal to

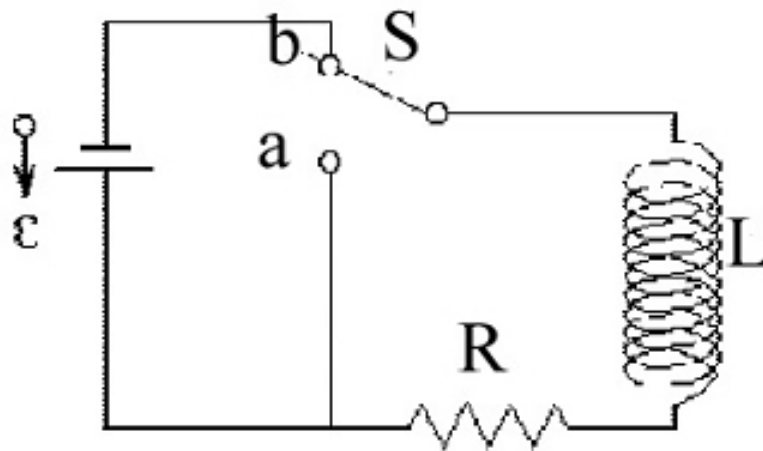1. \mathcal{E}/R
2. $\mathcal{E}/2R$
3. Zero
4. Don't have a clue



Consider an inductor connected to a battery with *emf* \mathcal{E} and a resistor R . The switch S has been in position b for a very long time. At $t = 0$, the switch is thrown to position a . The current I through the resistor for $t > 0$ is:

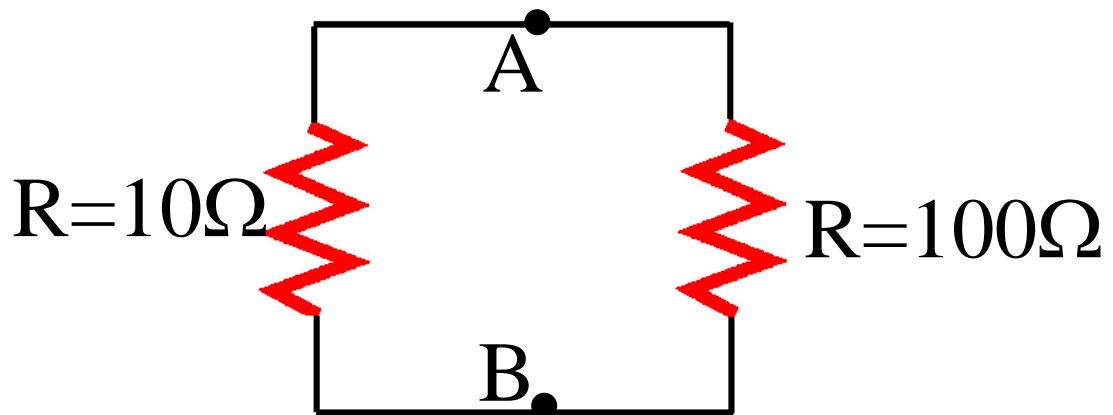1. $\frac{\mathcal{E}}{R}e^{-Rt/L}$
2. $\frac{\mathcal{E}}{R}\left(1 - e^{-Rt/L}\right)$
3. Zero
4. Don't have a clue



A magnetic field B penetrates this circuit outwards, and is increasing at a rate such that a current of 1 A is induced in the circuit (which direction?).

The potential difference $V_A - V_B$ is:

1. +10 V
2. -10 V
3. +100 V
4. -100 V
5. +110 V
6. -110 V
7. +90 V
8. -90 V
9. None of the above

Driving a Motor

Consider a motor (a loop of wire rotating in a B field) which is driven at a constant rate by a battery through a resistor.

Now grab the motor and prevent it from rotating. What happens to the current in the circuit?

1. Increases
2. Decreases
3. Remains the Same