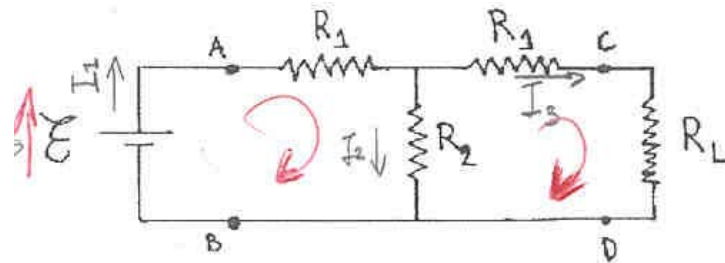


October 8, 2002  
Solutions for Practice Quiz #6

---

The emf source  $E$  is connected as shown in the figure below in a network that involves resistors  $R_1$ ,  $R_2$  and  $R_L$



Let us first introduce the arrows for  $I_1, I_2, I_3, \text{emf}$  and the "positive" direction in summing potentials. Notice that with the exception of the emf, all other directions are completely arbitrary. Flipping the "positive" direction in summing potentials on a loop simply changes the sign of both hand sides of an equation. For what concerns  $I_1, I_2$  and  $I_3$  though, if we end up with negative values, that means that our initial guess of the direction was wrong and instead the opposite one is the correct.

There are 3 loops that are formed of which 2 equations are independent. There is also a junction equation (charge conservation). There are three unknowns ( $I_1, I_2, I_3$ ) and we need three (independent) equations in order to determine them. Pick any 2 loop equations and the junction equation, follow Kirchhoff's laws and you are done.

$$\mathcal{E} - I_1 R_1 - I_2 R_2 = 0$$

$$\mathcal{E} - I_1 R_1 - I_3 R_1 - I_3 R_L = 0$$

$$I_1 = I_2 + I_3$$

Notice that there are 3 correct answers to this problem. Which are the other 2?

In calculating  $R_{\text{eff}}$ , proceed in steps identifying that you have the right most  $R_1$  in series with  $R_L$ . Their sum is in parallel with  $R_2$ . This sum is in series with the left most  $R_1$ .

$$R_{\text{eff}} = R_1 + \frac{(R_1 + R_L)R_2}{R_1 + R_L + R_2}$$

Equate the above  $R_{\text{eff}}$  with  $R_L$  to find out that:

$$R_{\text{eff}} = R_L \Rightarrow R_1^2 + \cancel{R_1 R_L} + \cancel{R_1 R_2} + \cancel{R_1 R_2} + \cancel{R_L R_2} = \cancel{R_1 R_L} + R_L^2 + \cancel{R_2 R_L}$$

$$\Rightarrow 2R_1 R_2 = R_L^2 - R_1^2 \Rightarrow R_2 = \frac{R_L^2 - R_1^2}{2R_1}$$

In order to find out  $V_{CD}$ , you should identify that  $I_1 = \text{emf}/R_{\text{eff}} = \text{emf}/R_L$  (remember,  $R_{\text{eff}} = R_L$ ) and  $I_3 = V_{CD}/R_L$ . You then have:

$$\mathcal{E} - I_1 R_1 - I_3 (R_1 + R_L) = 0 \Rightarrow \mathcal{E} - \frac{\mathcal{E}}{R_{\text{eff}}} R_1 - \frac{V_{CD}}{R_L} (R_1 + R_L) = 0 \Rightarrow$$

$$\mathcal{E} - \frac{\mathcal{E}}{R_L} R_1 - \frac{V_{CD}}{R_L} (R_1 + R_L) = 0 \Rightarrow \mathcal{E} (R_L - R_1) = V_{CD} (R_1 + R_L) \Rightarrow$$

$$V_{CD} = \mathcal{E} \frac{R_L - R_1}{R_L + R_1}$$