

8.022 (E&M) – Lecture 8

Topics:

- Electromotive force
- Circuits and Kirchoff's rules

Quiz 1: thoughts

- Average: 59, RMS: 16
 - Last year average: 64 → test slightly harder than average
 - Problem 1 had some subtleties + math looked scary
- When to worry
 - grade < 40: very serious danger, TEAL is strongly recommended
 - 40 < grade < 50: something is wrong, more work/changes needed
- The bottom line: 8.022 is a hard class
 - Fun (and useful) only if you are ready for it
 - If not, you may be better off with TEAL
- Prof. Kats and I are available for discussion/advise
 - Bring exam and psets with you
- Exams will be posted on the MIT server today at 12:30 PM

Last time


- Electric current I: $I = \frac{dQ}{dt}$
- Electric current density J: $\vec{J} \equiv qn\vec{u} \equiv \rho\vec{u}$
- Continuity equation: $\nabla \cdot \vec{J} + \frac{\partial \rho}{\partial t} = 0$
- Ohm's law:
 - Microscopic: $\vec{J} = \sigma \vec{E}$ Macroscopic: $V = IR$
 - σ =conductivity $\sigma = \frac{nq^2\tau}{m}$
 - R=resistance $R \equiv \frac{L}{\sigma A}$

EMF: Electromotive force

- What makes charges flow in circuits?
 - Potential difference ΔV
 - Source of charges
- This is what the EMF provides
 - NB: EMF=Electromotive force but it's not a force!!!
- Example of EMF: battery
 - Device that maintains separation of charges between 2 electrodes
 - Current flows inside via electrochemical reactions that produce ΔV

Car Battery

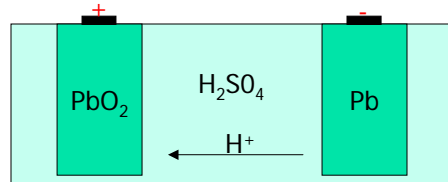- Two terminals (lead oxide PbO_2 and porous lead Pb) in sulfuric acid (H_2SO_4)




- When immersed in acid, Pb provides free electrons:

$$\text{Pb} + \text{HSO}_4^- \rightarrow \text{PbSO}_4 + \text{H}^+ + 2\text{e}^-$$
- At the lead oxide electrode, this reaction is energetically favored:

$$\text{PbO}_2 + 3\text{H}^+ + \text{HSO}_4^- + 2\text{e}^- \rightarrow \text{PbSO}_4 + 2\text{H}_2\text{O}$$
- If it is possible for both e^- and H^+ to travel from one terminal to the other:



Car Battery (2)

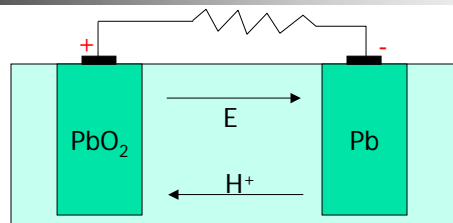

- When terminals are not connected: no flow of e⁻
- E in battery does not allow flow of H⁺ → inhibits reaction
- When terminals are connected: electrons start flowing freely
- Electric field is reduced → H⁺ can flow → reaction occurs

EMF of battery: $\phi(+ \text{ terminal}) - \phi(- \text{ terminal})$: ΔV available to drive circuit

$$EMF = \int_{- \text{terminal}}^{+ \text{terminal}} \vec{E} \cdot d\vec{s}$$

G. Sciolla – MIT


8.022 – Lecture 8

7

Convention

- We indicate EMF with this symbol:

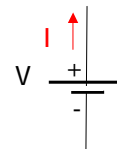- Long side: + terminal
- Short side: - terminal



- The current flows from + to –
 - Counterintuitive if you think about it in terms of electrons...


G. Sciolla – MIT

8.022 – Lecture 8

8

Kirchhoff' second rule

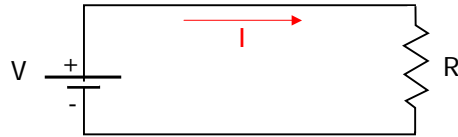- Close a battery on a resistor: simplest circuit!



- How much current flows in the circuit? Ohm's law: $I = \frac{V}{R}$
- When the current flows in a resistor there is a voltage drop $\Delta V = -IR$


Kirchhoff's second law:

Around any closed loops, the sum of EMF and potential drops is 0

- Equivalent to say that Electrostatic field is conservative: $\oint \vec{E} \cdot d\vec{s} = 0$

Solving circuits

- If we have more than 1 resistor:

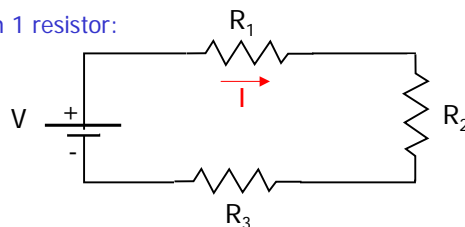

- Solve the circuit: determine currents and voltages everywhere
- What we know:
 - Current flowing in the circuit must be the same everywhere, or Q would accumulate somewhere
 - Voltage drop in the i^{th} resistor: $\Delta V_i = -IR_i$
 - Second Kirchhoff rule: $V - \sum_i V_i = 0$


$$V - \sum_{i=1,3} V_i = V - I \sum_{i=1,3} R_i = 0 \Rightarrow I = \frac{V}{R_1 + R_2 + R_3}$$

Resistors in series

- We implicitly derived an important result. We wrote:

$$V - \sum_{i=1,3} V_i = V - I \sum_{i=1,3} R_i = 0 \Rightarrow I = \frac{V}{R_1 + R_2 + R_3}$$

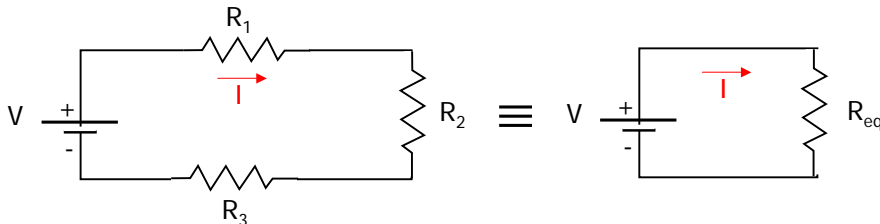- What does it mean? Same current flowing in these two circuits:




$$R_{eq} = \sum_i R_i$$

G. Sciolla – MIT

11

Solving circuits

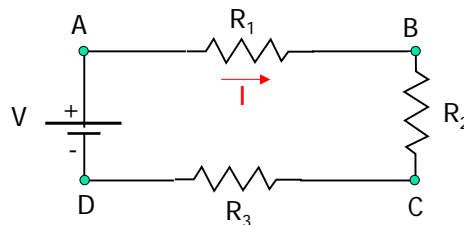- Solve the circuit: determine currents and voltages everywhere



- Calculate V_{AB} , V_{BC} , V_{CD} , V_{DA} , V_{AC} , ...

$$V_{AB} = IR_1 = \frac{VR_1}{R_1 + R_2 + R_3}; \quad V_{BC} = IR_2 = \frac{VR_2}{R_1 + R_2 + R_3}$$

$$V_{CD} = IR_3 = \frac{VR_3}{R_1 + R_2 + R_3}; \quad V_{AC} = I(R_2 + R_1) = \frac{V(R_1 + R_2)}{R_1 + R_2 + R_3}$$


G. Sciolla – MIT

8.022 – Lecture 8

12

Application (F13)

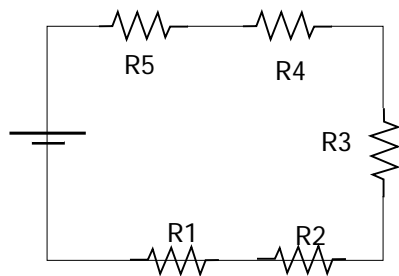- What is the resistance of electrical components?




Elements of the circuit:

- Saline solution
- Resistor
- Diod
- light bulb
- Fluorescent light

- How to measure knowing the current = 135 mV?
- You are given a voltmeter!

Kirchhoff's first rule

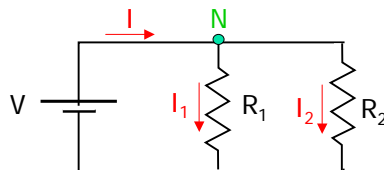- Let's now connect resistors in parallel:



- At the node N the current I divides up into 2 pieces: I_1 and I_2

Kirchhoff's first law:

At any node, sum of the currents in = sum of the currents out


- In other words: there is no accumulation of charges in the circuit

Kirchhoff's first rule: application

- Solve the circuit:

$$V = I_1 R_1 \Rightarrow I_1 = \frac{V}{R_1}$$
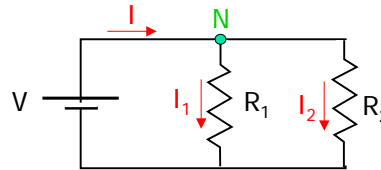
$$V = I_2 R_2 \Rightarrow I_2 = \frac{V}{R_2}$$



- Apply Kirchhoff's first law: $I = I_1 + I_2$


$$I = I_1 + I_2 = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

Resistors in parallel

- Again, we are learning something important. We said:

$$I = I_1 + I_2 = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

- What does it mean?

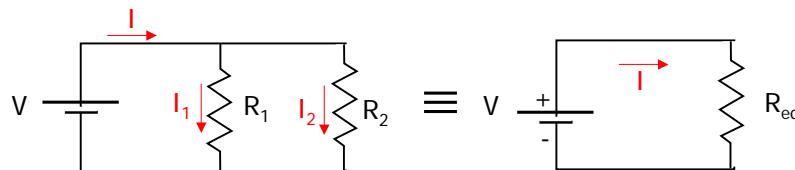


$$\frac{1}{R_{\text{eq}}} = \sum_i \frac{1}{R_i}$$

Resistors in parallel vs. in series

- Resistors in series:

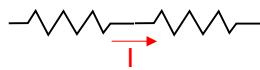
- The current flowing is one → add resistors → make the path harder
→ I decreases → R_{eq} increases → R_{eq} larger than any single resistor



$$R_{eq} = \sum_i R_i$$

- Resistors in parallel:

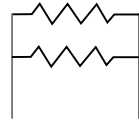- The current flows in many resistors → add resistors → make path easier
→ I increases → R_{eq} is smaller than any single resistor



$$\frac{1}{R_{eq}} = \sum_i \frac{1}{R_i}$$


G. Sciolla – MIT

8.022 – Lecture 8


17

Application (F12)

- Consider the two circuits:

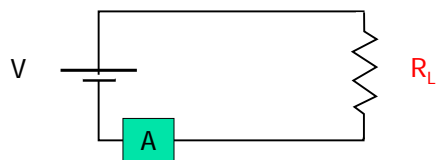

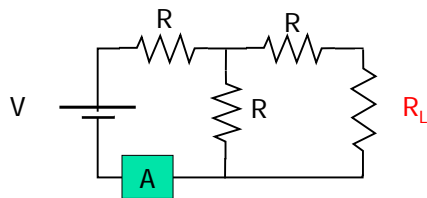$V = 1.5 \text{ V}$
 $R_L = 1580 \Omega$
 Ammeter reading: 0.94 mA



$R_L = 1580 \Omega$
 $R = 912 \Omega$
 Ammeter reading: ?? mA


G. Sciolla – MIT

8.022 – Lecture 8

18

Slightly harder circuits

- How do we solve this?

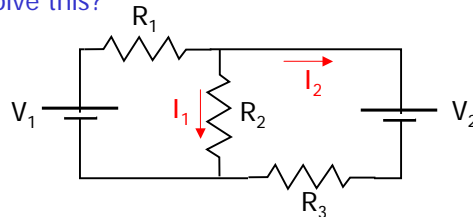


- Reducing the circuit does not work:
 - Series and parallels won't work
 - Because of second EMF
- But Kirchhoff still holds so:
 - Apply First Kirchhoff law to each node
 - Apply Second Kirchhoff law to each loop

Slightly harder circuits (2)

- Solution:

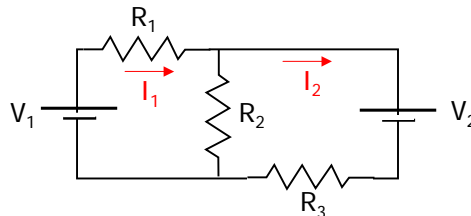- Left loop:
 - $V_1 - I_1 R_1 - (I_1 - I_2) R_2 = 0$
- Right loop:
 - $-V_2 - I_2 R_3 - (I_2 - I_1) R_2 = 0$
- Node:
 - $I(\text{in } R_2) = I_1 - I_2$



- Solving the system:

$$I_1 = \frac{V_1 R_3 + (V_1 - V_2) R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$


$$I_2 = \frac{(V_1 - V_2) R_2 + V_2 R_1}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

How to go through a loop?

- Assign current direction (arbitrary)
- Choose a path (clockwise or ACW)
- EMF: >0 when $- \rightarrow +$ and <0 when $+ \rightarrow -$
- V always drops on R

Internal resistance

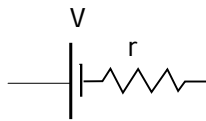- When battery delivers current to circuit there is a flow of current in the battery itself.
 - In previous example this current comes from flux of H^+ ions
- The chemical reaction will dissipate energy, battery gets hot, energy that could have gone in the circuit is lost
 - This is equivalent to having a resistor r inside the battery:



- Corollary:
There is a max current the battery can generate: $I_{\max} = V/r$
- Homework:
Short a little battery with a wire and see how hot it gets: careful! ☺

Power dissipated in resistors

- When current flows in circuit, it moves charges through $\Delta V \rightarrow$ work
- Work done to drive a charge dq through a potential difference V :

$$dW = Vdq$$

- If work is done in time $dt \rightarrow$ the power dissipated is:

$$P = \frac{dW}{dt} = V \frac{dq}{dt} = VI$$

- When Ohm's law hold:

$$P = VI = RI^2$$

- Units: $[P] = [\text{Energy}]/[\text{time}]$

- cgs: erg/s
- SI: J/s

Power is important: it's what does work in a circuit: how much light is produced, how much heat, etc.

Dependence of R on T (F16)

- Ohm's law tells us that $V=RI$
- This is valid in any resistor
- Does it mean that given a voltage I is constant over time?
- Not necessarily!
 - When I goes through R it dissipates power $=RI^2$
 - $R=f(T) \rightarrow R$ is not constant while resistor heats up!
- Last time: increase $T \rightarrow$ increase $R \rightarrow$ decrease I
- Pulse a light bulb with a saw tooth voltage:
What do you expect to observe?
As the filament warms up, R changes
 \rightarrow the slope of I vs V changes over time

Summary and outlook

- Today:
 - First look at circuits: Kirchhoff's laws
 - Resistors in series and parallel
 - Power dissipated in resistors
- Next time:
 - RC circuits and evolution of currents over time
- Remember: come and talk to us today if test < 50
 - Make appointment by email is safer
 - Add date is THIS FRI!!!